

---

**Development of RF hardware using STM32WB microcontrollers**

---

**Introduction**

STM32WB Series microcontrollers integrate a high quality RF transceiver for Bluetooth® Low Energy and 802.15.4 radio solution.

Special care is required for the layout of an RF board compared to a conventional circuit.

At high frequencies copper interconnections (traces) behave as functional circuit elements introducing disturbances that can degrade RF performance. Parasitic components created by traces and pads contribute significantly to the overall circuit behavior. Layout rules have to be carefully followed to mitigate these effects and achieve the requested performance.

This document describes the precautions to be taken to achieve the best performance from the MCU. The description is based on the QFN48 / QFN68 / UFBGA129 reference boards for 2-layer PCBs, and on the WLCSP100 reference board for the 4-layer PCB.

For some products of the STM32WB Series only QFN48 is available, check the product datasheet available on [www.st.com](http://www.st.com).

These guidelines are generic, they need to be adapted to the specific application.

# Contents

<b>1</b>	<b>RF basics</b>	<b>6</b>
1.1	Terminology	6
1.1.1	Power	6
1.1.2	Gain	6
1.1.3	Loss	6
1.1.4	Reflection coefficient, voltage standing wave ratio and return loss	6
1.1.5	Harmonics	7
1.1.6	Spurious	7
1.1.7	Intermodulation	7
1.2	Impedance matching	7
1.3	Smith chart	7
1.3.1	Normalized impedance	8
1.3.2	Reading a Smith chart	8
<b>2</b>	<b>Reference board schematics</b>	<b>12</b>
<b>3</b>	<b>Components choice</b>	<b>17</b>
3.1	Capacitor	17
3.2	Inductor	18
3.3	SMPS	19
3.4	External crystal	20
<b>4</b>	<b>PCB stack and technology</b>	<b>21</b>
4.1	RF transmission lines	21
4.2	PCB substrate choice	21
4.3	2-layer PCB	22
4.4	4-layer PCB	23
<b>5</b>	<b>Layout recommendations</b>	<b>25</b>
5.1	2-layer PCB	25
5.2	4-layer PCB	27
5.3	Critical parts	28
5.3.1	RF	28

---

	5.3.2	SMPS .....	30
	5.3.3	LSE .....	31
<b>6</b>		<b>Reference boards with IPD .....</b>	<b>32</b>
<b>7</b>		<b>Conclusion .....</b>	<b>36</b>
<b>8</b>		<b>Revision history .....</b>	<b>37</b>

List of tables

Table 1. External components ..... 12

Table 2. Capacitor temperature ranges ..... 18

Table 3. 2-layer PCB - Reference values ..... 22

Table 4. 4-layer PCB - Reference values ..... 24

Table 5. References ..... 32

Table 6. Document revision history ..... 37



## List of figures

Figure 1.	Smith chart . . . . .	8
Figure 2.	Series connection . . . . .	9
Figure 3.	Smith chart for admittance . . . . .	9
Figure 4.	Parallel connection . . . . .	10
Figure 5.	Smith chart with impedance and admittance . . . . .	10
Figure 6.	Smith chart with VSWR circles . . . . .	11
Figure 7.	Adapting a network with the Smith free SW . . . . .	11
Figure 8.	UFQFPN48 reference board . . . . .	13
Figure 9.	VFQFPN68 reference board . . . . .	14
Figure 10.	UFBGA129 reference board . . . . .	15
Figure 11.	WLCSP100 reference board . . . . .	16
Figure 12.	Capacitor equivalent circuit . . . . .	17
Figure 13.	Capacitor impedance vs. frequency . . . . .	17
Figure 14.	Inductor equivalent circuit . . . . .	18
Figure 15.	Inductor impedance vs. frequency . . . . .	19
Figure 16.	Connection of an external crystal . . . . .	20
Figure 17.	Coplanar waveguide (CPW) . . . . .	21
Figure 18.	2-layer PCB . . . . .	22
Figure 19.	2-layer PCB - Reference boards for UFQFPN48, VFQFPN68 and UFBGA129 . . . . .	22
Figure 20.	4-layer PCB . . . . .	23
Figure 21.	4-layer PCB - Reference board for WLCSP100 . . . . .	24
Figure 22.	PCB layout for UFQFPN48 (left to right: all, top and bottom layers) . . . . .	25
Figure 23.	PCB layout for VFQFPN68 (left to right: all, top and bottom layers) . . . . .	25
Figure 24.	PCB layout for UFBGA129 . . . . .	26
Figure 25.	PCB layout for WLCSP100 . . . . .	27
Figure 26.	Detail of PCB layout for the RF . . . . .	29
Figure 27.	Detail of PCB layout for the SMPS . . . . .	30
Figure 28.	Detail of PCB layout for the LSE . . . . .	31
Figure 29.	Different matching networks (discrete components on the left, IPD on the right) . . . . .	32
Figure 30.	RF performance of the MLPF-WB55-01E3 . . . . .	33
Figure 31.	RF performance of the MLPF-WB55-02E3 . . . . .	33
Figure 32.	IPD package (bumpless CSP) . . . . .	34
Figure 33.	PCB layout with discrete matching network (left) and with IPD (right) . . . . .	35

# 1 RF basics

This section covers generic terms and definitions used in RF board design.

The following references can help the user.

1 Paul Horowitz and Winfield Hill	The art of electronics (3 <sup>rd</sup> edition)	Cambridge University Press
2 Roger C. Palmer	An introduction to RF circuit design for communication systems (2 <sup>nd</sup> edition)	Newnes
3 Christopher Bowick	RF circuit design (2 <sup>nd</sup> edition)	Newnes
4 Joseph J. Carr and George W. Hippisley	Practical antenna handbook (5 <sup>th</sup> edition)	McGraw-Hill Education
5 Smith chart (free SW)		<a href="http://www.fritz.dellsperger.net">http://www.fritz.dellsperger.net</a>
6 Coplanar waveguide calculator (free SW)		<a href="http://wcalc.sourceforge.net">http://wcalc.sourceforge.net</a>

## 1.1 Terminology

### 1.1.1 Power

This unit, expressed in dBm, is the measure of the RF signal strength: **dBm = 10 Log P**, where P is the power in mW. So it will be:

- 1 pW = -90 dBm
- 10 µW = -20 dBm
- 1 mW = 0 dBm
- 2 mW = 3 dBm
- 10 mW = 10 dBm

### 1.1.2 Gain

The gain (expressed in dB) is the ratio between the output and the input power of an RF device. Negative values correspond to an attenuation.

### 1.1.3 Loss

If there is impedance mismatch, incorrect transmission line design or incorrect PCB material selection between two stages of a circuit, signal power losses appear and not all the power is transmitted from one stage to the following one. There are also inherent losses, e.g. the dielectric loss, which depends upon the laminate and materials used to manufacture the board.

### 1.1.4 Reflection coefficient, voltage standing wave ratio and return loss

When a signal flows from a source to a load via a transmission line, if there is a mismatch between the characteristic impedance of the transmission line and the load a portion of the

signal will be reflected back to the source. The polarity and the magnitude of the reflected signal depend on whether the load impedance is higher or lower than the line impedance.

The reflection coefficient ( $\Gamma$ ) is the measure of the amplitude of the reflected wave versus the amplitude of the incident wave, namely  $\Gamma = (Z - Z_0) / (Z + Z_0) = (z - 1) / (z + 1)$ .

The voltage standing wave ratio (VSWR) is the measure of the accuracy of the impedance matching at the point of connection. It is a function of the reflection coefficient and is expressed as  $VSWR = (1 + |\Gamma|) / (1 - |\Gamma|)$ . If VSWR is 1, there is no reflected power.

The return loss (RL) is a function of the reflection coefficient, but expressed in dB:  
 $RL = 20 \log |\Gamma|$ .

### 1.1.5 Harmonics

The harmonics are the integer unwanted multiples of input frequency (fundamental frequency).

### 1.1.6 Spurious

The spurious are the non-integer multiples of input frequency (unwanted frequencies).

### 1.1.7 Intermodulation

When two RF signal are mixed together, intermodulation products are the signals composed by an integer multiple of the sum and the difference between the two signals.

## 1.2 Impedance matching

To optimize the RF performance it is imperative to adapt the impedance matching from the antenna to the input of the chip, as well as that from the chip output to the antenna.

If this adaptation is poor, it will introduce losses in the RX/TX chain. These losses will immediately translate in lower sensitivity and in lower signal amplitude of the transmitted signal. These disadaptpations, if high enough, will increase the level of TX harmonics.

As a consequence it is very important to spend efforts to adapt as best as possible the RF chain. In the Bluetooth® Low Energy bandwidth of the STM32WB, and more generally in RF frequencies, spurious elements (such as PCB track inductances and layer capacitors, trace length) have a significant impact on the impedance matching. To achieve the best TX/RX budget (optimum transfer of signal and energy) between the load and the STM32WB, a dedicated matching network is needed between the two blocks.

The maximum power is transferred when the internal resistance of the source equals the resistance of the load. When extended to a circuit with a frequency-dependent signal, to obtain maximum power transfer the load impedance must be the complex conjugate of the source impedance.

## 1.3 Smith chart

The Smith chart ([Figure 1](#)) is used to determine the matching network.

### 1.3.1 Normalized impedance


The normalized impedance  $z$  is a complex impedance ( $r$  is the real part and  $x$  the imaginary part):  $z = r + jx = Z / Z_0$  where  $Z_0$  is the characteristic impedance and is often a constant (in our case  $Z_0 = 50 \Omega$ ).

For a capacitor  $z = -j / (2 \pi * f * C * Z_0)$ , for an inductor  $z = j (2 \pi * f * L) / Z_0$ .

### 1.3.2 Reading a Smith chart

The Smith chart is represented with the normalized impedance scale  $z = Z / Z_0$ .

Figure 1. Smith chart

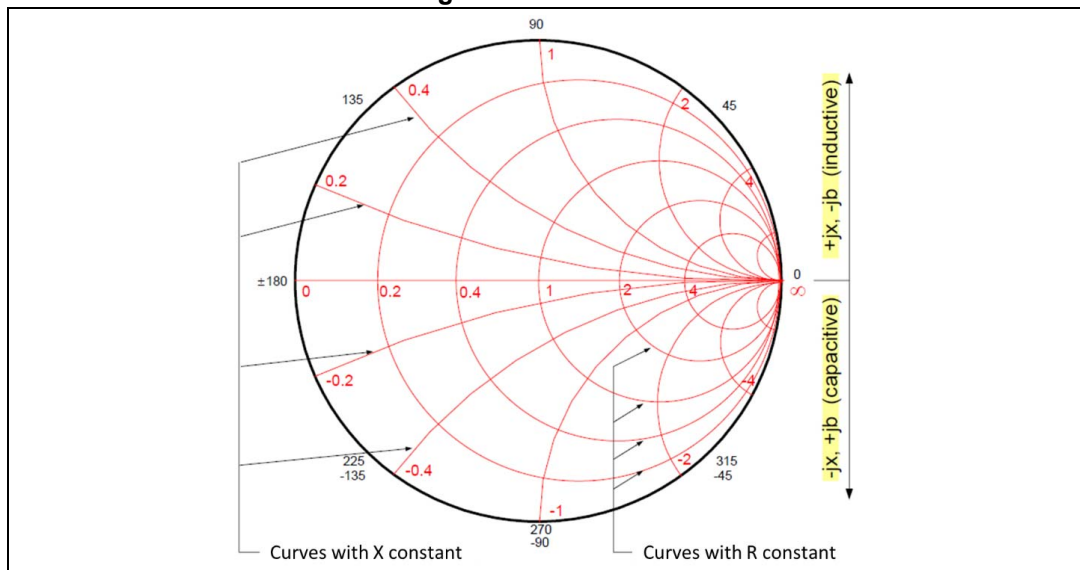

If  $Z_0 = 50 \Omega$ , when there is matching ( $Z = Z_0$ ) the normalized impedance at  $50 \Omega$  is 1 and it is the center of the Smith chart. The goal in the search of a matching network is to converge towards this point.

The horizontal axis of the Smith chart represents pure resistors: at the left side,  $z = 0$  (short circuit) and at the right side,  $z = \infty$ .

The region located above the X axis represents impedances with inductive reactance (positive imaginary part of the complex impedance) or capacitive susceptance (positive imaginary part of the complex admittance).


The region below the X axis represents impedances with capacitive reactance (negative imaginary part of the complex impedance) or inductive susceptance (negative imaginary part of the complex admittance).

#### Serial inductor or capacitor

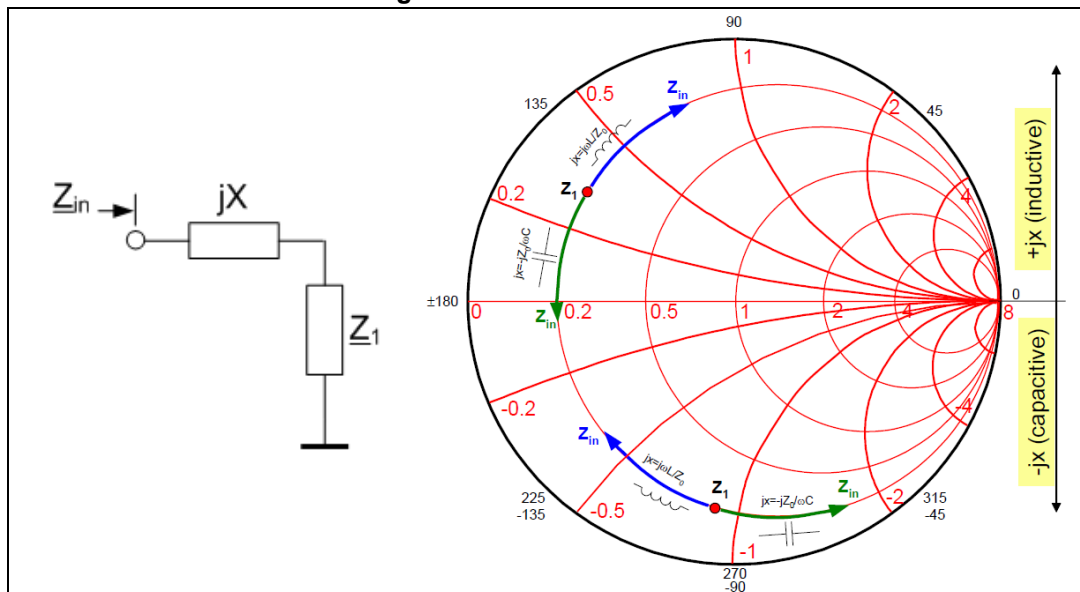If an inductor or a capacitor is in series with the load impedance  $Z_1$  the resulting impedance  $Z_{in}$  moves as shown in [Figure 2](#).

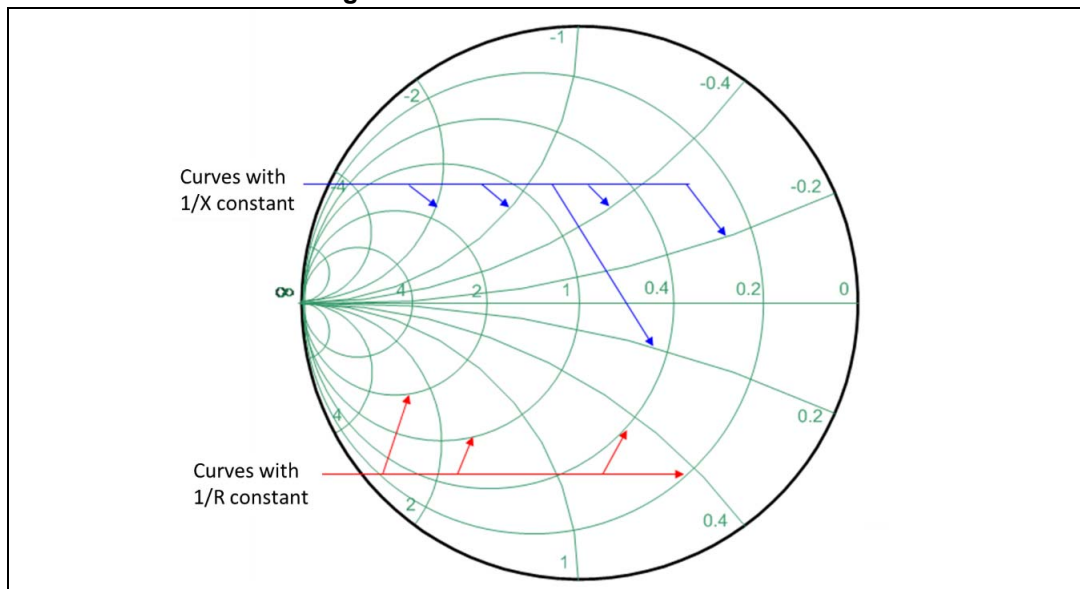


Figure 2. Series connection



As for the Smith chart in normalized impedance ( $z$ ) scale, the Smith chart can be represented in normalized admittance ( $y = 1/z$ ) scale as shown in [Figure 3](#).


Figure 3. Smith chart for admittance



### Parallel inductor or capacitor


If an inductor or a capacitor is in parallel with the load admittance  $Y_1$  the resulting impedance  $Y_{in}$  moves as shown in [Figure 4](#).

Figure 4. Parallel connection

 

In [Figure 5](#) the Smith chart in impedance and admittance planes.

Figure 5. Smith chart with impedance and admittance

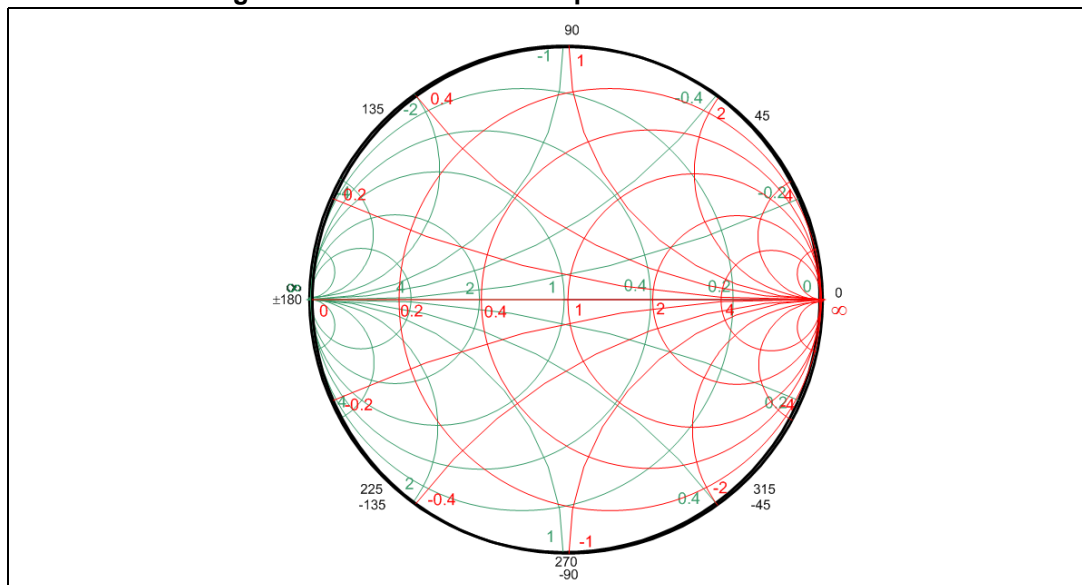

The circles with constant VSWR are an additional information can be retrieved from the Smith chart even when they are not represented. These circles have the same center, and as values the intersections between the circle and the right side of the horizontal axis from the center (see [Figure 6](#)).

Figure 6. Smith chart with VSWR circles


 


Figure 7 is an example of the free software “Smith”: starting from  $Z_L = (25.00 - j*8.00) \Omega$ , represented on the Smith chart by DP1, the goal is to obtain  $Z_{in} = 50 \Omega$ . By adding (in series or in parallel) inductors or capacitors, the impedance converges towards the center of the graph.

Figure 7. Adapting a network with the Smith free SW

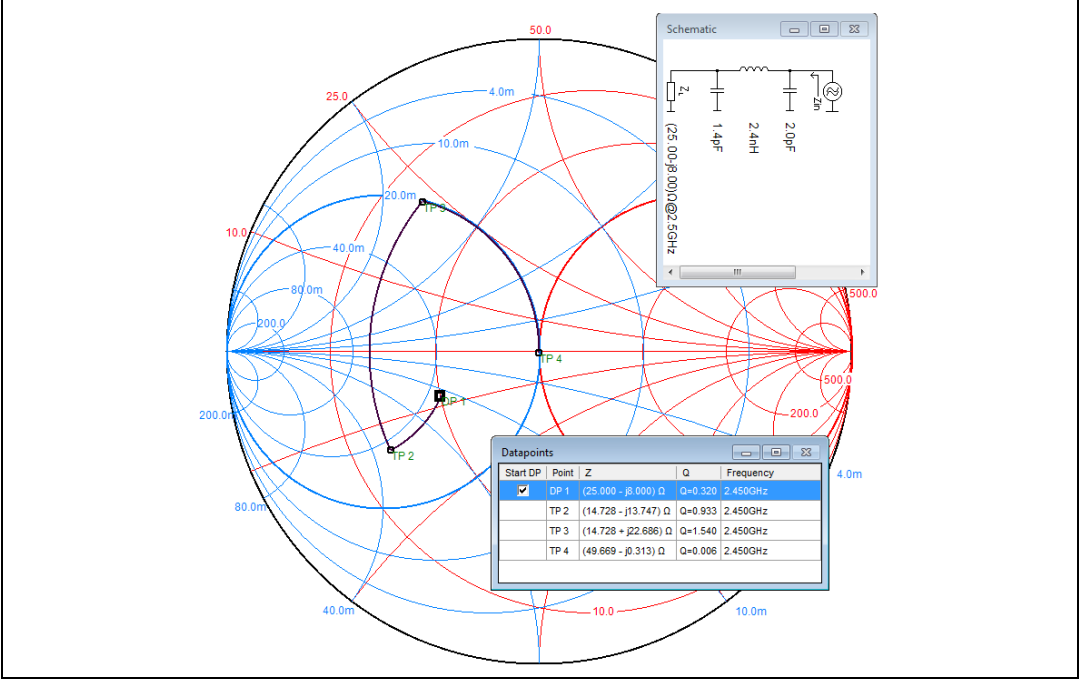

## 2 Reference board schematics

The STM32WB Series microcontrollers are based on Arm<sup>®(a)</sup> cores.

The schematics in [Figure 8](#), [Figure 9](#) and [Figure 10](#) represent, respectively, the 2-layer reference boards for UFQFPN48, VFQFPN68 and UFBGA129 packages. [Figure 11](#) represents the 4-layer reference board for WLCSP100. The RF output is only from SMA. All the layout guidelines described in the next paragraphs for two layers PCB are based on these boards.

**Table 1. External components**

Component(s)	Description
C1, C2	Decoupling capacitors for $V_{DDRF}$
C3, C4	Matching capacitors
C5, C6, C7	Decoupling capacitors for $V_{DD}$
C8	Decoupling capacitor for $V_{BAT}$
C9	Decoupling capacitor for $V_{DDUSB}$
C10	Decoupling capacitor for $V_{DDA}$
C12	Decoupling capacitor for SMPS
C11, C13	DC-DC converter filtering capacitors
C14, C15	X2 capacitors
C16	Decoupling capacitor for NRST pin
D1	Diode protection for NRST pin
FLT1	Integrated Low-Pass Filter
L1	Matching inductor
L2, L3	DC-DC converter inductor
L4	Filtering inductor for $V_{DDA}$
R1	Pull-up resistor for NRST
R2	Boot selector resistor
U1	STM32WBxx
X1	High frequency crystal
X2	Low frequency crystal

arm

a. Arm is a registered trademark of Arm Limited (or its subsidiaries) in the US and/or elsewhere.

Figure 8. UFQFPN48 reference board

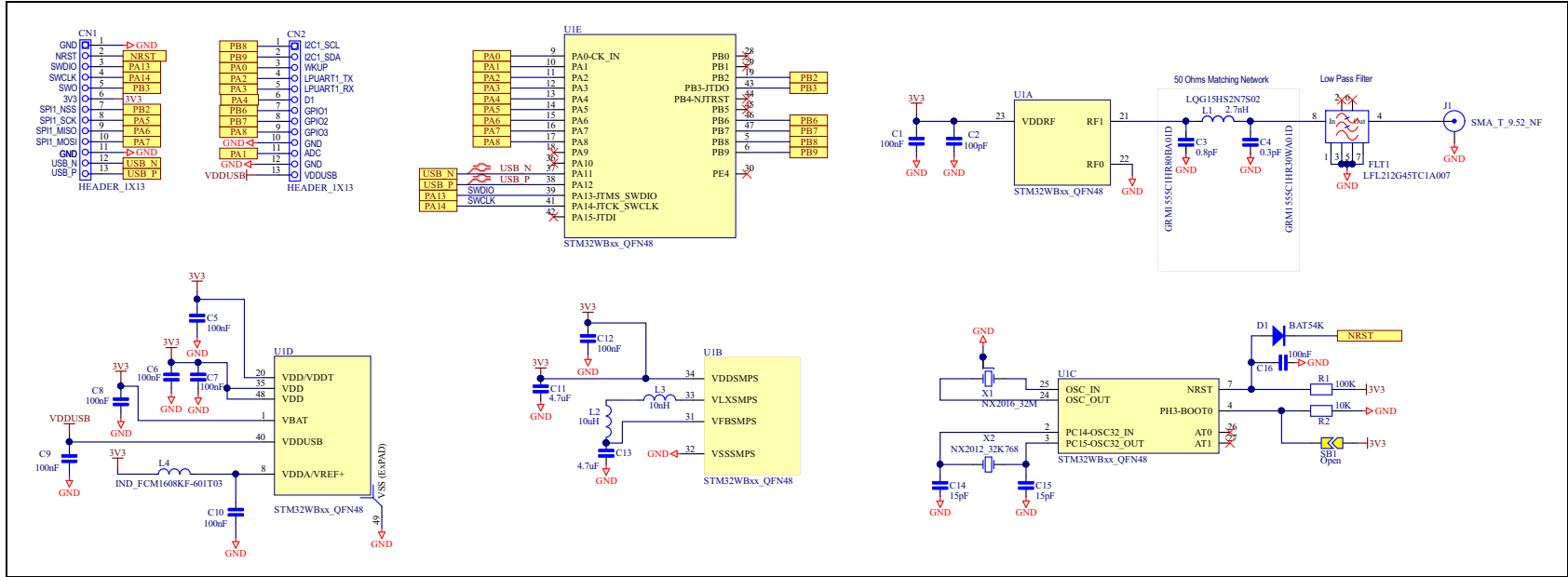


Figure 9. VFQFPN68 reference board


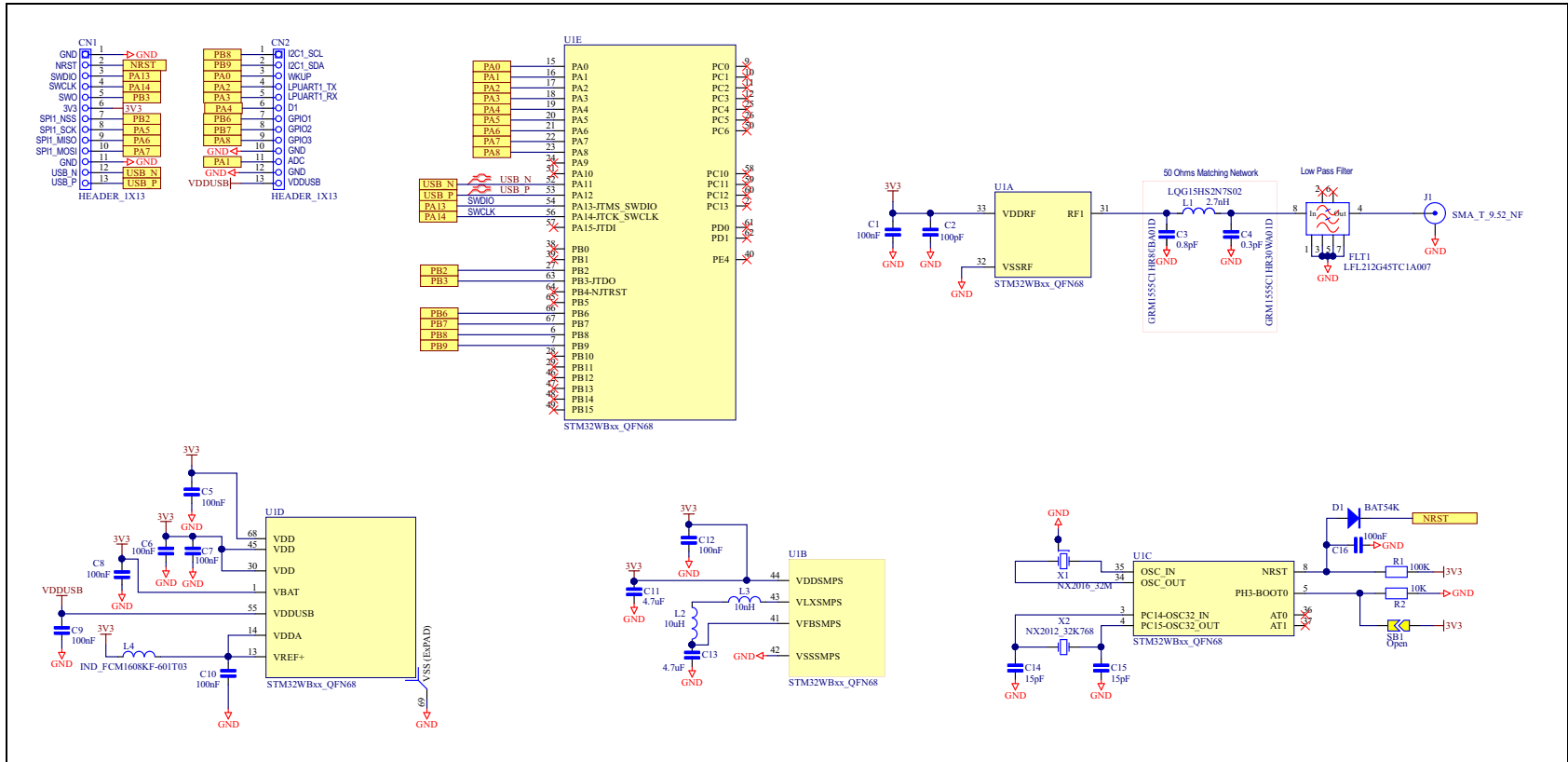


Figure 10. UFBGA129 reference board

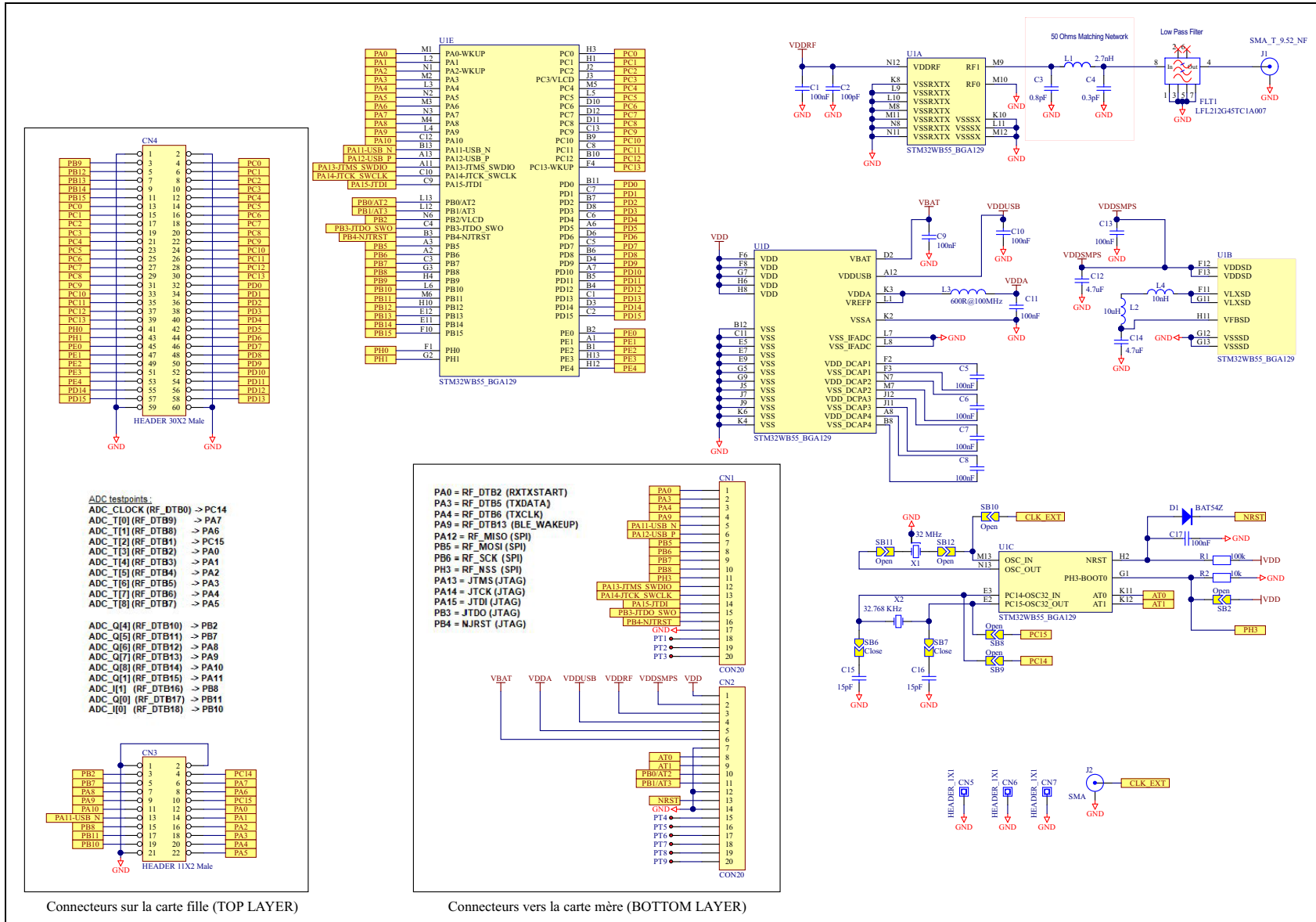

The image displays a complex PCB layout for an STM32WBxx\_CSP100 module. The layout includes several key components and their connections:

- Connectors:** CN1 (Header\_1X13), CN2 (Header\_1X13), J1 (SMA\_T\_9.52\_NF), J2 (NX2012\_32M), J3 (NX2012\_32K768), J4 (BAT54K), J5 (IND\_FCM1608KF-601T03).
- Capacitors:** C1 (100nF), C2 (100pF), C3 (1.5pF), C4 (1.0pF), C5 (100nF), C6 (100nF), C7 (100nF), C8 (100nF), C9 (100nF), C10 (100nF), C11 (4.7uF), C12 (100nF), C13 (4.7uF), C14 (15pF), C15 (15pF).
- Inductors:** L1 (2.2nH), L2 (10uH), L3 (10nH), L4 (100nH).
- Integrated Circuits (ICs):**
  - U1A:** STM32WBxx\_CSP100, VDDRF, VSSRF, SWCLK, SWIO.
  - U1B:** STM32WBxx\_CSP100, VDDSMPS, VLXSMPS, VFBSMPS, VSSSMPS.
  - U1C:** STM32WBxx\_CSP100, OSC\_IN, OSC\_OUT, PH3-BOOT0, AT0, AT1.
  - U1D:** STM32WBxx\_CSP100, VBAT, VDDUSB, VDDA, VREF+, VSSA/VREF-.
- Other Components:** R1 (100K), R2 (10K), R3 (10K), R4 (10K), R99 (10K), R100 (10K).

The layout is organized into several sections, with components labeled with their respective values and connections. The overall design is a detailed representation of the hardware for the STM32WBxx\_CSP100 module.



### 3 Components choice

In the Bluetooth® Low-Energy bandwidth and more generally at high frequencies, the choice of the external components is critical because they directly influence the performance of the application.

#### 3.1 Capacitor

A capacitor is a passive electrical component used to store energy in an electrical field. They are made with different construction techniques, materials (such as double-layer, polyester, polypropylene) and sizes. For RF design, it is recommended to use ceramic capacitors on surface mount version.

The equivalent circuit of a capacitor is represented in [Figure 12](#). The resistor  $R_p$  represents its leakage current, while  $R_s$  is the equivalent serial resistor (ESR) and represents all ohmic losses of the capacitor. The inductor  $L_s$  is the equivalent serial inductance (ESL) and its value is function of the SRF (self-resonant frequency). From [Figure 13](#) it can be appreciated that the impedance of the capacitor is capacitive at low frequencies, at the SRF is resistive, and inductive at higher frequencies.

Figure 12. Capacitor equivalent circuit


 


Figure 13. Capacitor impedance vs. frequency

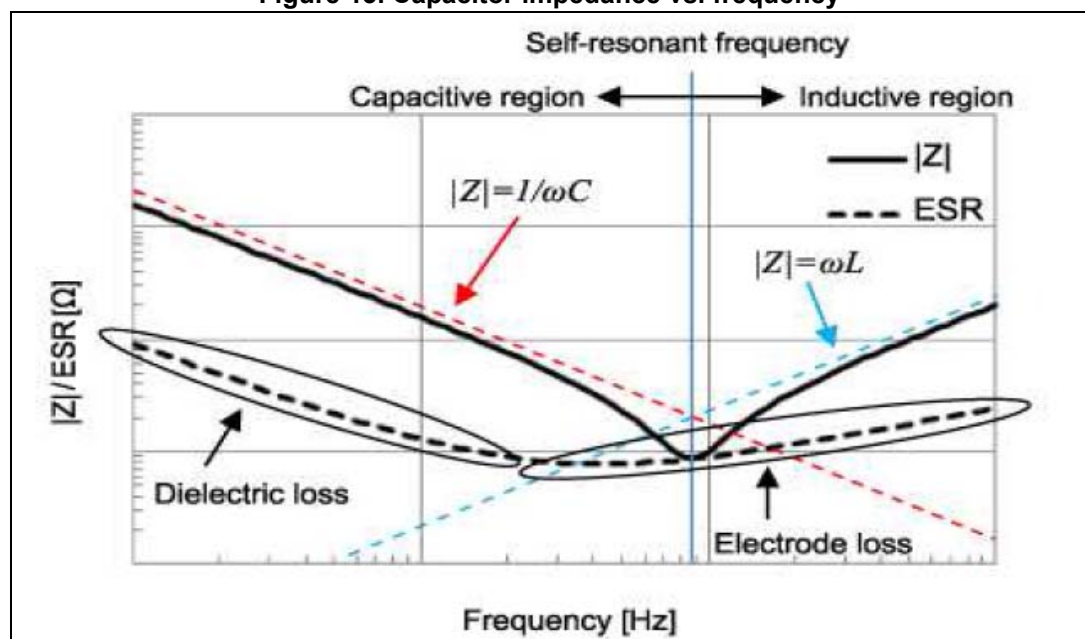

For RF matching, multilayer ceramic capacitors offer linear temperature coefficients, low losses and stable electrical properties over time, voltage and frequency. SMD (Surface Mount Device) is used with a 0402 package, which is a good compromise between performance and handling.

For RF decoupling, the capacitance value must be chosen so that the frequency to be decoupled is close to or just above the self-resonant frequency of the capacitor.

For DC-DC converter, as the quality factor of a capacitor is inversely proportional to its ESR, a capacitor with low insertion loss and a good quality factor is recommended. The capacitor requires either an X7R or X5R dielectric.

Table 2. Capacitor temperature ranges

Minimum temperature		Maximum temperature		Variation over the temperature range	
Code	Temperature	Code	Temperature	Code	Variation (%)
X	-55 °C (-67 °F)	4	+65 °C (+149 °F)	P	±10
		5	+85 °C (+185 °F)	R	±15
Y	-30 °C (-22 °F)	6	+105 °C (+221 °F)	S	±22
		7	+125 °C (+257 °F)	T	+22 / -33
Z	+10 °C (+50 °F)	8	+150 °C (+302 °F)	U	+22 / -56
		9	+200 °C (+392 °F)	V	+22 / -82


### 3.2 Inductor

An inductor is a passive electrical component used to store energy in its magnetic field. Inductors differ from each other for construction techniques and materials used to manufacture.

For RF design, where a high Q (Quality factor =  $\text{Im}[Z] / \text{Re}[Z]$ ) is required to reduce insertion loss, it is generally recommended to use air core inductors. Those inductors do not use a magnetic core made of ferromagnetic material, but are wound on plastic, ceramic, or another nonmagnetic material. SMD is also used with a 0402 package.


The equivalent circuit of an inductor is shown in [Figure 14](#). The resistor  $R_s$  represents the losses due to the winding wire and terminations, its value increases with temperature. The resistor  $R_p$  represents the magnetic core losses, it varies with frequency, temperature and current. The capacitor  $C_p$  is associated with the windings.

Figure 14. Inductor equivalent circuit

 

As shown in [Figure 15](#), at SRF the impedance and inductance are at their maximum. At lower / higher frequencies impedance and inductance increase / decrease with frequency.

**Figure 15. Inductor impedance vs. frequency**

 

For RF matching and decoupling, a good compromise between application cost and RF performance is to use an inductor with medium Q.

For DC-DC converter, the nominal value is 10  $\mu\text{H}$ . The inductor value affects the peak-to-peak ripple current, the output voltage ripple and the efficiency. The selected inductor has to be rated for its DC resistance and saturation current.

It is important to use the components shown in the schematics to obtain the best RF performance with the given PCB layout of the reference boards.

### 3.3 SMPS

Some STM32WBxx microcontrollers (check the product datasheet available on [www.st.com](http://www.st.com)) embed an SMPS (switched mode power supply) that can be used to improve power efficiency when  $V_{DD}$  is high enough.

In order not to disturb the RF performances, this SMPS has its switching frequency synchronous with the RF main clock source HSE. The allowed frequency for the SMPS are 4 or 8 MHz. Note that during RF startup phases from low power modes, the HSI will be used instead of HSE, to allow a faster wakeup time than waiting from the HSE stabilization before starting the SMPS and the Digital logic.

Two specific features have been added to this step down SMPS in association with all the low power modes supported by the STM32WB microcontrollers:

To operate properly the SMPS needs two inductors and two capacitors, whose value depend upon the targeted performance, and upon the PCB area and total height allowed in the mechanical design.

For best power performances, 4 MHz should be selected, leading to a 10  $\mu\text{H}$  inductor associated with a 4.7  $\mu\text{F}$  bulk capacitance. For smaller footprint, and especially to use very

low profile inductor, the 8 MHz can be selected, making it possible to use a 2.2  $\mu\text{H}$  inductor associated with a 4.7  $\mu\text{F}$  bulk capacitance.

For all packages it is advised to add an extra 10 nH inductor in series with the 10 or 2.2  $\mu\text{H}$  one, to filter the RF harmonic that can degrade the receiver performance.

Another 4.7  $\mu\text{F}$  capacitor must be used to decouple the  $V_{\text{DDSMPS}}$  supply. All of these external components must have the lowest possible ESR values. Note that  $V_{\text{DDSMPS}}$  must be connected to  $V_{\text{DD}}$ , and that voltage rising and falling must satisfy the conditions described in the STM32WB data sheet.

### 3.4 External crystal

Two oscillators with external crystals are available on the STM32WB microcontrollers.

The HSE (High Speed External) with 32 MHz frequency is used by the RF subsystem. The crystal X1 has to be placed as close as possible to the oscillator pins OSC\_IN and OSC\_OUT to minimize output distortion and start-up stabilization time. The load capacitances are integrated on chip and can be tuned according to the selected crystal via an internal register. By default, the load capacitances are 8 pF for the NX2016 from NDK used on the boards.


The LSE (Low Speed External) with 32.768 kHz frequency is used for the RTC subsystem.  $C_1$  and  $C_2$  values must be tuned to meet to the recommended load capacitance  $C_0$  of the selected crystal. Low power consumption and fast start-up time are achieved with a low  $C_0$  value. On the contrary, a higher  $C_0$  leads to a better frequency stability.

With reference to [Figure 16](#), the total load capacitance  $C_0$  seen by the crystal is  

$$C_0 = [(C_1 + C_{\text{PAD}} + C_{\text{PB1}}) * (C_2 + C_{\text{PAD}} + C_{\text{PB2}})] / (C_1 + C_{\text{PAD}} + C_{\text{PB1}} + C_2 + C_{\text{PAD}} + C_{\text{PB2}})$$
 where:

- $C_{\text{PAD}}$  accounts for the parasitic capacitance of the STM32WB pads, of the SMD components  $C_1$  and  $C_2$ , and of the crystal itself.
- $C_{\text{PB1}}$  and  $C_{\text{PB2}}$  represent the PCB routing parasitic capacitances. They must be minimized by placing X2,  $C_1$  and  $C_2$  close to the chip, thus improving the robustness against noise injection.
- $C_1$  and  $C_2$  must be connected to ground by a separate via.

Figure 16. Connection of an external crystal

 

## 4 PCB stack and technology

PCB traces at RF frequencies have to be designed carefully because their length is a fraction of the signal wavelength. Furthermore, the impedance of a PCB trace at RF frequencies depends on the thickness of the trace, its height above the ground plane, and the dielectric constant and loss tangent of the PCB dielectric material. Another important parameter is the PCB stack up, described in this paragraph.


RF boards are usually designed with at least two or four layers to obtain the best performance.

### 4.1 RF transmission lines

The transmission lines on a PCB can be implemented on external layers (microstrips and coplanar waveguides), or buried in internal layers (striplines).

The coplanar waveguide (CPW) transmission line is composed (see [Figure 17](#)) of a central signal line of width  $W$  between two ground planes, separated from them by a gap  $G$ . The central line and ground planes are on the surface of a dielectric substrate of a thickness  $H$ .

Figure 17. Coplanar waveguide (CPW)

 

A version of CPW named GCPW or CPWG exists, with a ground plane opposite to the dielectric.


### 4.2 PCB substrate choice

There are different types of PCB substrate, even if built with the same basic material (glass), some of them have controlled parameters that are more suitable for RF product. The PCB substrate used in RF designs is FR-4 (flame resistant 4). This material is known to retain its high mechanical values and electrical insulating qualities in both dry and humid conditions, at the expenses of dielectric constant stability over frequency and loss.

### 4.3 2-layer PCB

With the 2-layer PCB (see [Figure 18](#)), the RF signals and routing are on the top layer while the bottom layer is used for grounding under the RF zones, and for routing in others parts. The ground plane must be continuous under the RF zones, otherwise the return path current can increase and degrade the RF performance.


**Figure 18. 2-layer PCB**

 

The 2-layer PCB provides a cheaper solution and can provide performance equivalent to those of the 4-layer PCB, but requires careful signal routing and component placement.

The 2-layer PCB definition of the reference boards for the UFQFPN48, VFQFPN68 and UFBGA129 packages is shown in [Figure 19](#) and the values are summarized in [Table 3](#).

**Figure 19. 2-layer PCB - Reference boards for UFQFPN48, VFQFPN68 and UFBGA129**

 

**Table 3. 2-layer PCB - Reference values**

Parameter	Symbol	Value	Tolerance
Coating thickness above copper (soldermask)	T1(C)	10 to 18 $\mu\text{m}$	$\pm 5 \mu\text{m}$
Coating thickness above substrate (soldermask)	T2(C)	$\geq 10 \mu\text{m}$	$\pm 5 \mu\text{m}$
Dielectric coating (soldermask)	$\epsilon_r(\text{C})$	3.4	$\pm 0.1$
Trace thickness L1 (Cu + plating)	T1(T)	29.3 $\mu\text{m}$	$< 6 \mu\text{m}$
Substrate height L1/L2	H1(S)	1.47 mm	$\pm 10\%$
Dielectric substrate L1/L2	$\epsilon_{r1}(\text{C})$	4.2	$\pm 0.1$
Trace thickness L2 (Cu + plating)	T2(T)	29.3 $\mu\text{m}$	$< 6 \mu\text{m}$
Width error of trace	We(T)	12.7 $\mu\text{m}$	$> 8 \mu\text{m}$
Minimum trace width	Wt_min(T)	0.05 mm	$\pm 20\%$

Table 3. 2-layer PCB - Reference values (continued)


Parameter	Symbol	Value	Tolerance
Minimum isolation width	$W_{t_{min}}(T)$	0.01 mm	$\pm 20\%$
Minimum hole diameter	$D_{min}(HS)$	0.2 mm	$\pm 0.05$ mm
Minimum via diameter	$D_{min}(VS)$	0.3 mm	$\pm 0.05$ mm

## 4.4 4-layer PCB

With the 4-layer PCB shown in [Figure 20](#), it is recommended to have the following distribution:

- TOP layer: RF signal and routing on the top layer
- INNER1 layer: routing the others parts
- INNER2 layer: power and low frequency routing, ground reference under RF zone(s)
- BOTTOM layer: low frequency routing

Figure 20. 4-layer PCB

 

The 4-layer PCB solution is more complicated and expensive. The laser-filled and the buried vias have to be used to connect the tracks to the internal balls.

The 4-layer PCB definition of the reference board for the WLCSP100 is shown in [Figure 21](#) and the values are summarized in [Table 3](#).

Figure 21. 4-layer PCB - Reference board for WLCSP100

 


Table 4. 4-layer PCB - Reference values

Parameter	Symbol	Value	Tolerance
Coating thickness above copper (soldermask)	T1(C)	10 to 18 $\mu\text{m}$	$\pm 5 \mu\text{m}$
Coating thickness above substrate (soldermask)	T2(C)	$\geq 10 \mu\text{m}$	$\pm 5 \mu\text{m}$
Dielectric coating (soldermask)	$\epsilon_r(\text{C})$	3.4	$\pm 0.1$
Trace thickness L1 (Cu + plating)	T1(T)	29.3 $\mu\text{m}$	$< 6 \mu\text{m}$
Substrate height L1/L2	H1(S)	1.25 mm	$\pm 10\%$
Dielectric substrate L1/L2	$\epsilon_{r1}(\text{C})$	4.2	$\pm 0.1$
Trace thickness L2 (Cu + plating)	T2(T)	30 $\mu\text{m}$	$< 6 \mu\text{m}$
Substrate height L2/L3	H1(S)	1.14 mm	$\pm 10\%$
Dielectric substrate L2/L3	$\epsilon_{r2}(\text{C})$	4.2	$\pm 0.1$
Trace thickness L3 (Cu + plating)	T2(T)	30 $\mu\text{m}$	$< 6 \mu\text{m}$
Substrate height L3/L4	H1(S)	1.25 mm	$\pm 10\%$
Dielectric substrate L3/L4	$\epsilon_{r3}(\text{C})$	4.2	$\pm 0.1$
Trace thickness L4 (Cu + plating)	T2(T)	29.3 $\mu\text{m}$	$< 6 \mu\text{m}$
Width error of trace	We(T)	12.7 $\mu\text{m}$	$> 8 \mu\text{m}$
Minimum trace width	Wt <sub>min</sub> (T)	0.05 mm	$\pm 20\%$
Minimum isolation width	Wt <sub>min</sub> (T)	0.01 mm	$\pm 20\%$
Minimum hole diameter	D <sub>min</sub> (HS)	0.2 mm	$\pm 0.05 \text{ mm}$
Minimum via diameter	D <sub>min</sub> (VS)	0.3 mm	$\pm 0.05 \text{ mm}$



## 5 Layout recommendations

### 5.1 2-layer PCB

Figure 22. PCB layout for UFQFPN48 (left to right: all, top and bottom layers)

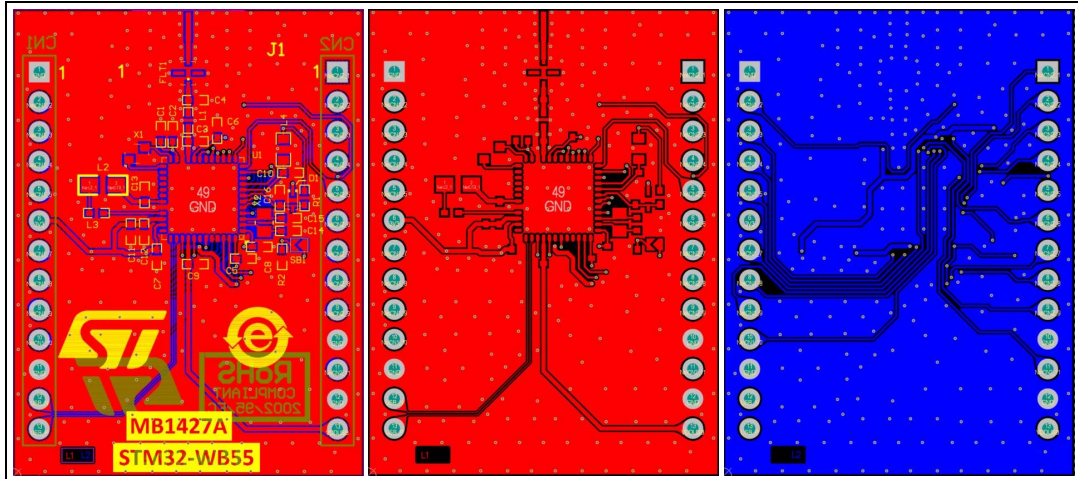


Figure 23. PCB layout for VFQFPN68 (left to right: all, top and bottom layers)



 


Figure 24. PCB layout for UFBGA129

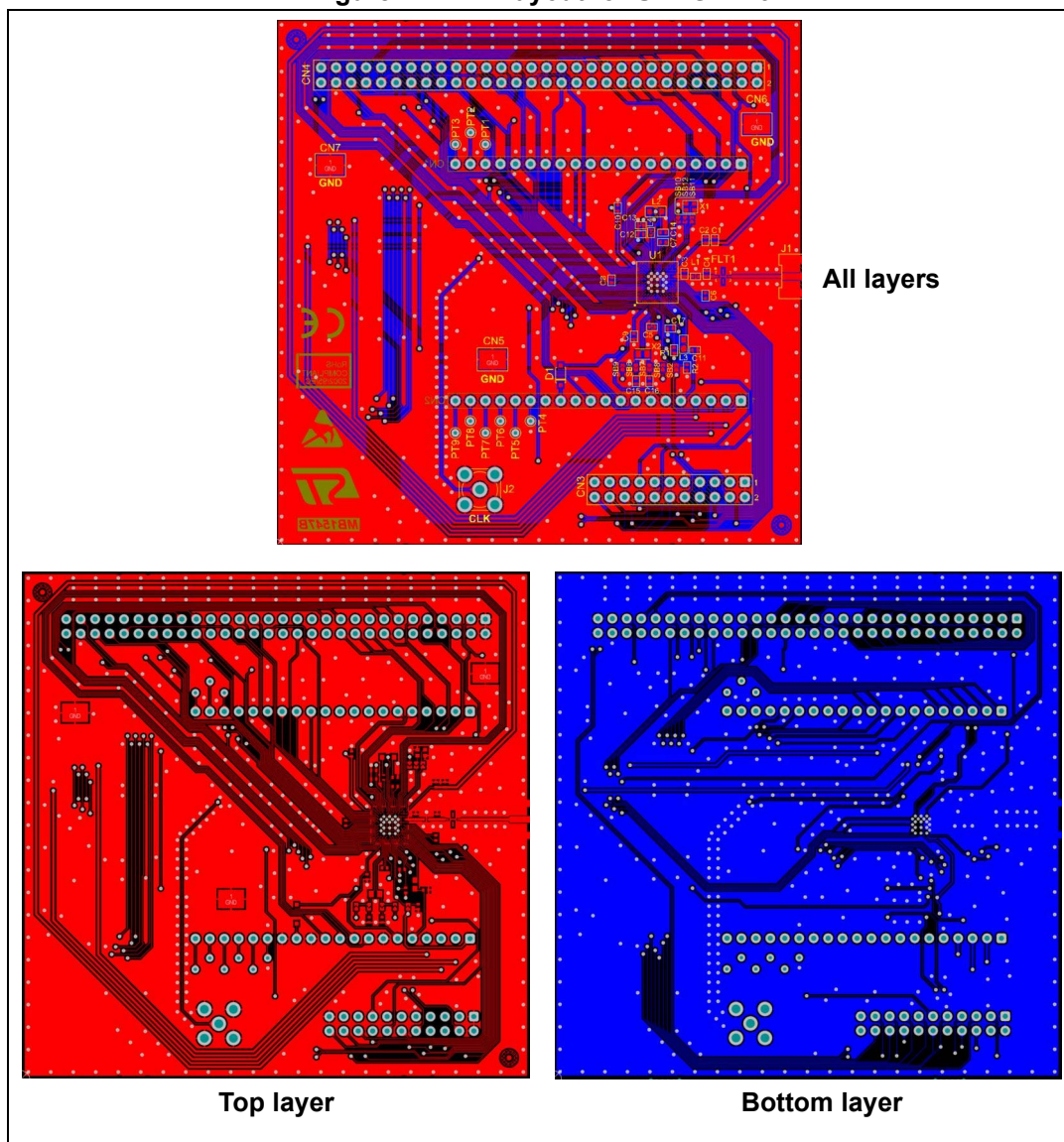

## 5.2 4-layer PCB

**Figure 25. PCB layout for WLCSP100**

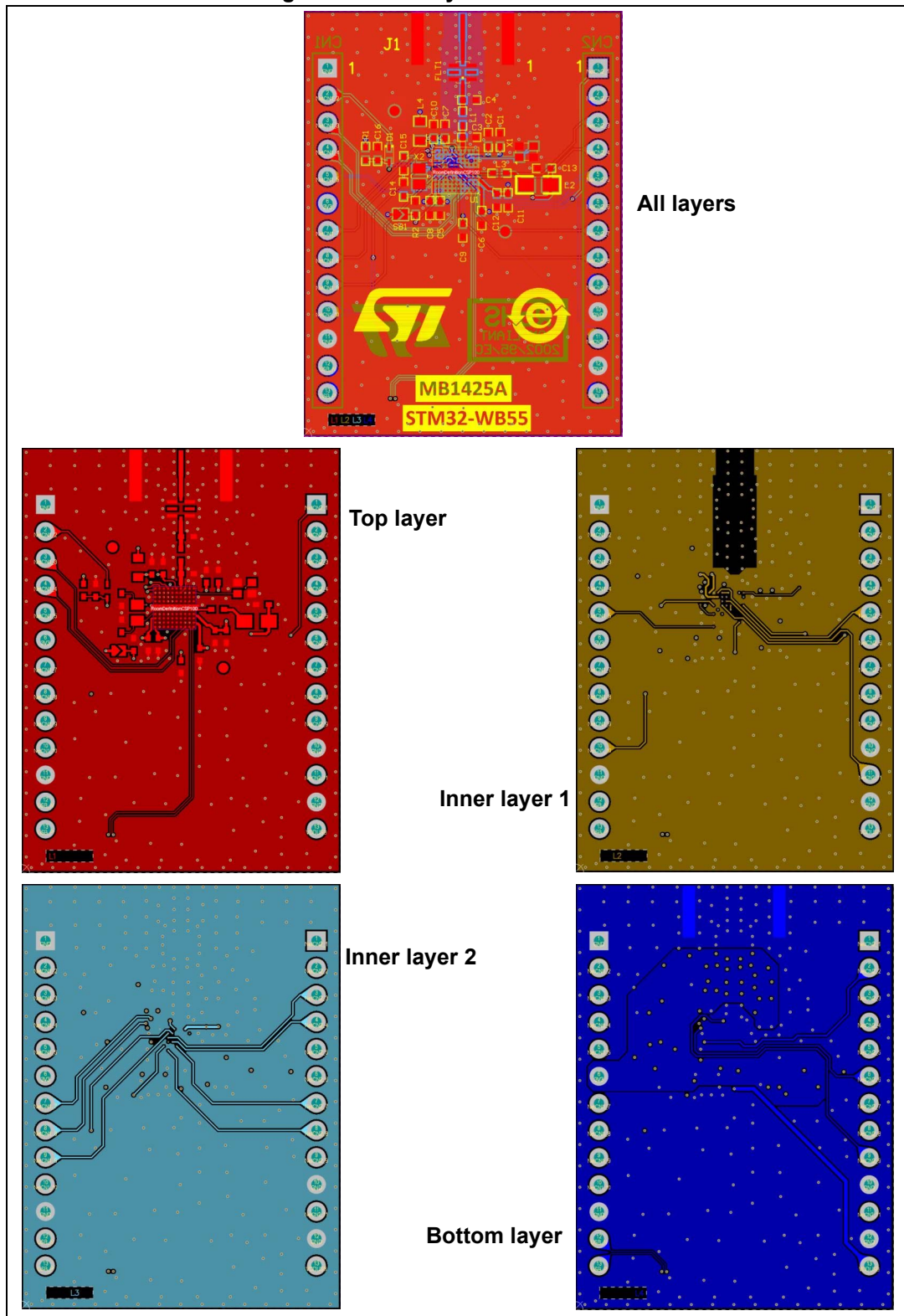

## 5.3 Critical parts

The three critical parts in the layout are the RF, the SMPS and the LSE.

### 5.3.1 RF

To obtain the best RF performance (in particular the maximum transmission power, the optimum reception sensitivity and a sufficient spurious and harmonic rejection), a matching network is required between the RF1 output pin and the RF low-pass filter.


This network is composed by a discrete LC PI filter followed by an integrated low-pass filter. C3 and L1 have the role of adapting the RF pin impedance of the STM32WB to 50  $\Omega$ , the impedance that must be seen by the SMA. C4 and the integrated low-pass filter FLT1 are used to reject the harmonic frequencies. The values of C3, C4 and L1 depend on the reference board PCB definition, detailed in [Section 2: Reference board schematics](#).

The low-pass filter FLT1 used has a mark to distinguish the direction. Respect the direction indicated on the PCB (the filter structure is not perfectly symmetric, the properties change with the mounting direction).

It is also recommended to place the matching network as near as possible to the RF output and to avoid long track between each component of this matching network. The track between the output of the low-pass filter FLT1 and the SMA connector can have a variable length, depending upon the application, provided that its impedance is always 50  $\Omega$ .




Figure 26. Detail of PCB layout for the RF

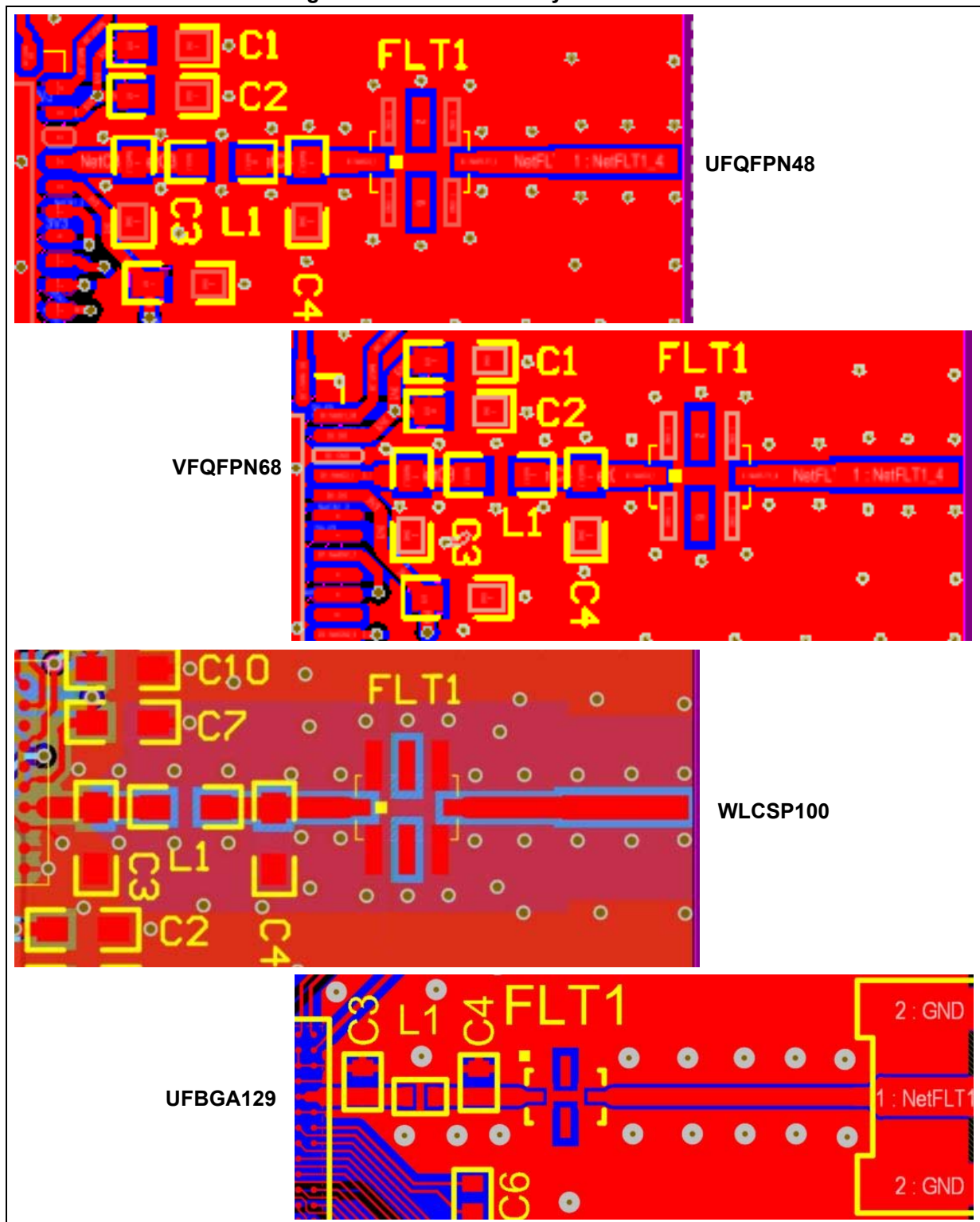

### 5.3.2 SMPS

In addition to the recommendations given in [Section 3.3: SMPS](#), to avoid important current loop when the STM32WB is in SMPS mode, it is recommended to place C11, C12 and C13 as close as possible to their respective pins on STM32WB. Do not forget to connect the solder pad to ground to have a strong current return path.


Figure 27. Detail of PCB layout for the SMPS

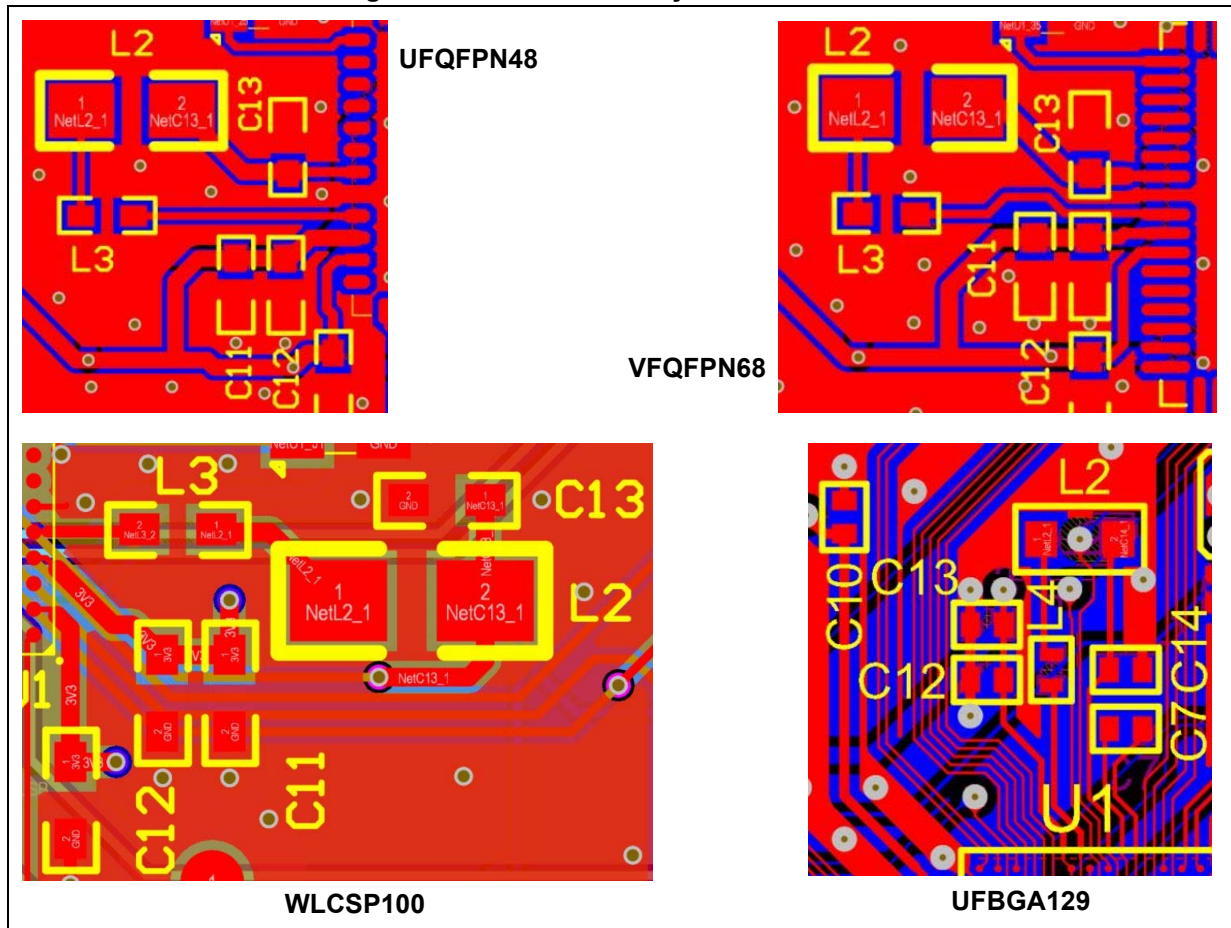

### 5.3.3 LSE

As indicated in [Section 3.4: External crystal](#), place X2, C14 and C15 as close as possible to their respective pins.


Figure 28. Detail of PCB layout for the LSE

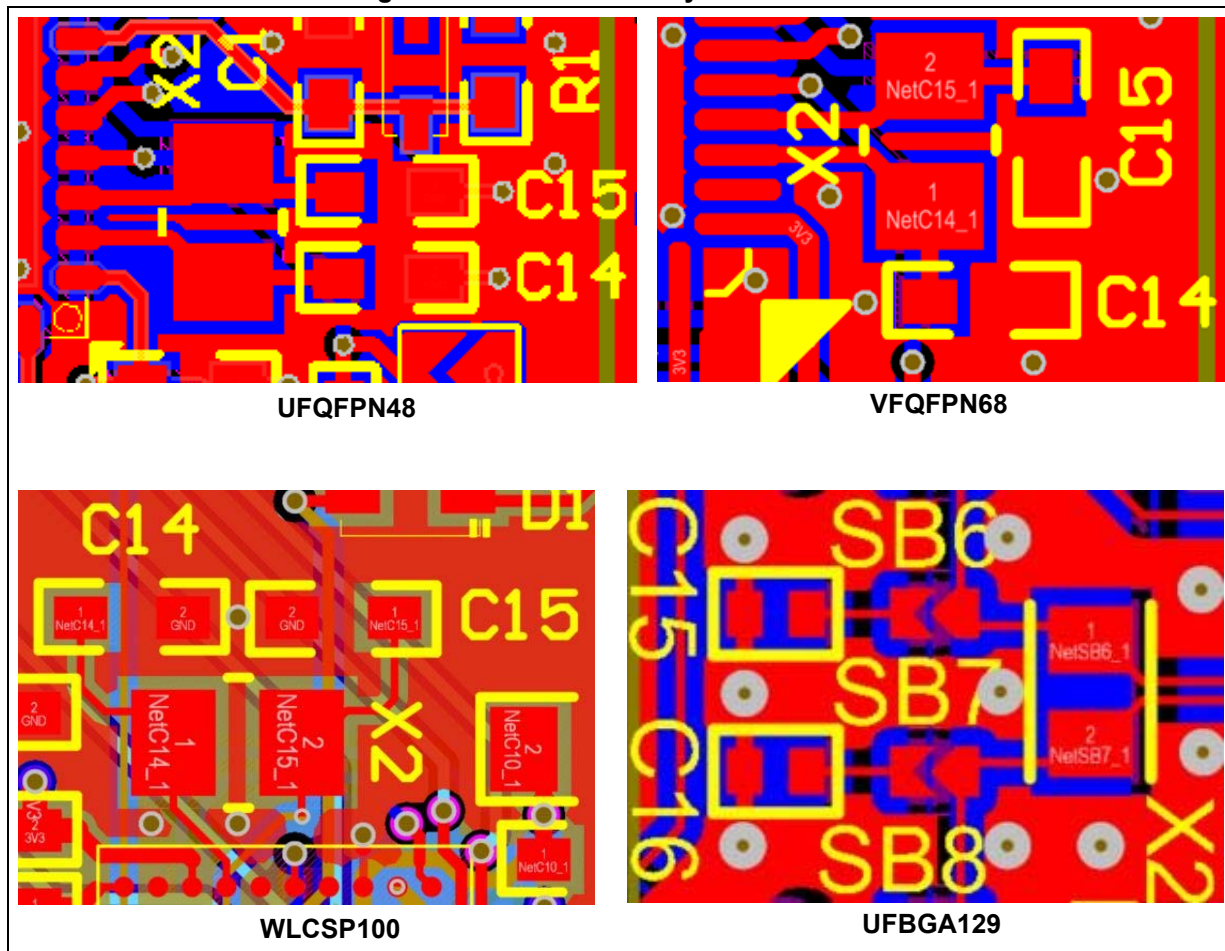

# 6 Reference boards with IPD

The goal of the IPD (integrated passive device) is to replace the discrete matching network plus the integrated low-pass filter keeping equivalent TX/RX performance. [Figure 29](#) shows the differences between the two approaches, using as example the QFN48 package.

**Figure 29. Different matching networks (discrete components on the left, IPD on the right)**

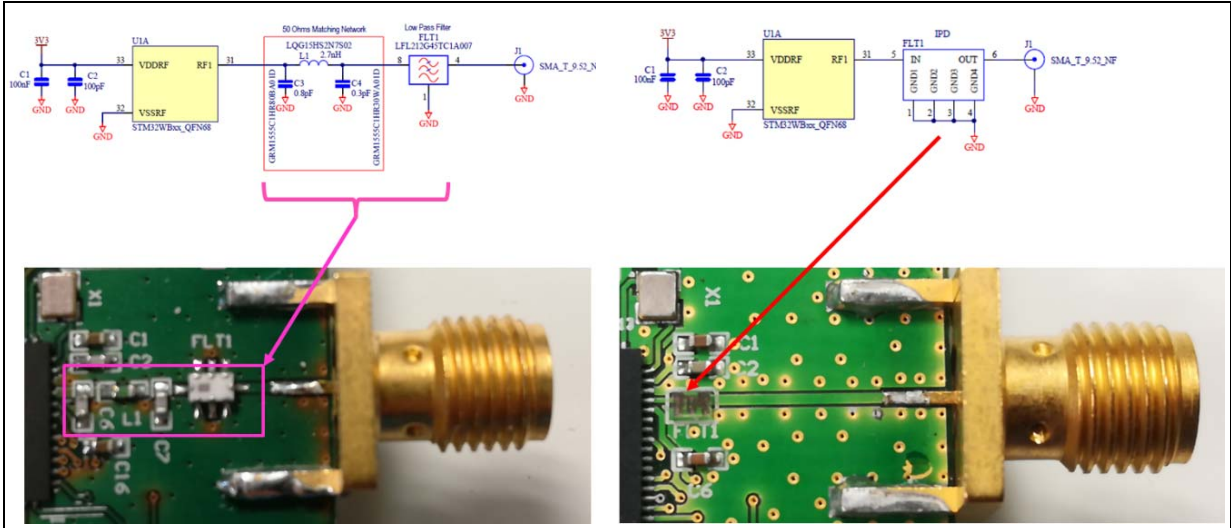

**Table 5. References**


Package	IPD reference	Document
QFN48	MLPF-WB55-01E3	DS12804 <sup>(1)</sup> , 2.4 GHz low pass filter matched to STM32WB55Cx/Rx
QFN68		
UFBGA129		
WLCSP100	MLPF-WB55-02E3	DS13176 <sup>(1)</sup> , 2.4 GHz low pass filter matched to STM32WB55Vx

1. Available on [www.st.com](http://www.st.com).




Transmission and insertion loss performance are shown, respectively, on the left and on the right side of [Figure 30](#) (MLPF-WB55-01E3) and of [Figure 31](#) (MLPF-WB55-02E3).

**Figure 30. RF performance of the MLPF-WB55-01E3**

 


**Figure 31. RF performance of the MLPF-WB55-02E3**

 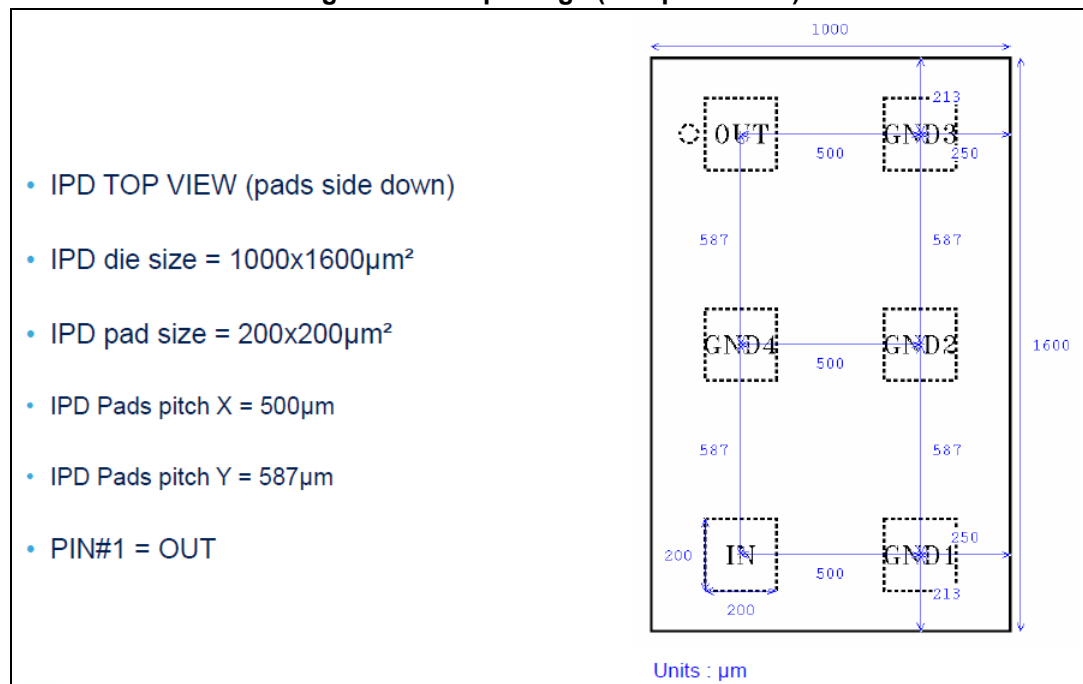


The bottom view of the IPD package is shown in [Figure 32](#).

**Figure 32. IPD package (bumpless CSP)**



The PCB can be greatly simplified, as shown in [Figure 33](#).

**Figure 33. PCB layout with discrete matching network (left) and with IPD (right)**

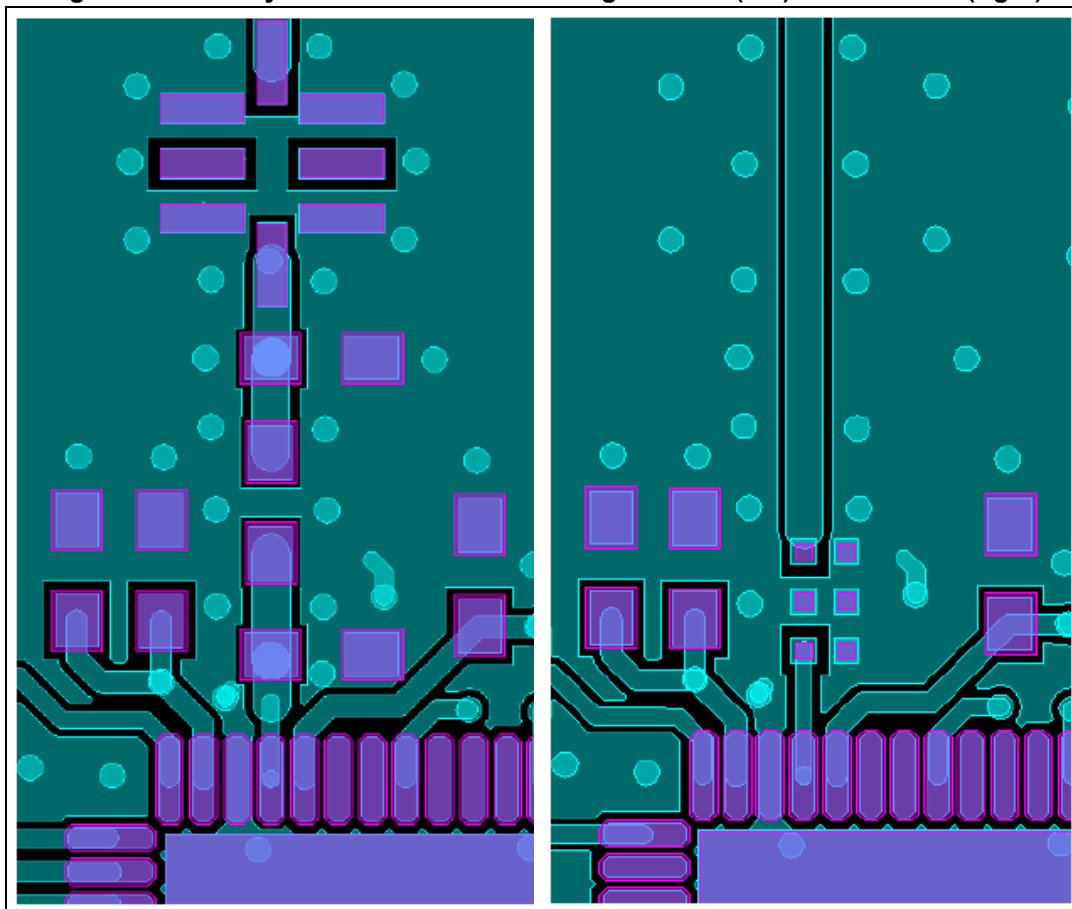

Note that the length of the track between the output of the IPD and the RF output can be further reduced to decrease the dimensions of the PCB. This improves RF performance by reducing losses due to the length of this track.

As a conclusion, the IPD reference MLPF-WB55-01E3 can replace the RF output network of the STM32WB for the QFN packages (an antenna filter is still needed) for a 2-layer PCB. The PCB size and the bill of materials will be reduced, while guaranteeing equivalent RF performance compared with the discrete RF output network. Another advantage of the IPD solution is the performance stability on volume production (lower parameter dispersion compared with the discrete components).

## 7 Conclusion

The STM32WB Series microcontrollers integrate a high performance RF front end.

To achieve the best TX and RX performance, several aspects have to be addressed during the PCB design:

- choice of the PCB technology (number of layers, substrate technology)
- computation of the antenna matching and filtering network
- floor plan and critical RF component placement and routing
- placement of the SMPS and LSE components (if used)

This application note provides useful guidelines to help the user to reach the performance specified in the datasheets.

## 8 Revision history

**Table 6. Document revision history**

Date	Revision	Changes
14-Sep-2018	1	Initial release.
18-Jan-2019	2	Added <a href="#">Section 6: Reference boards with IPD</a> .
28-Jan-2019	3	Changed document classification, from ST restricted to public.
24-Sep-2019	4	Updated <a href="#">Introduction</a> and <a href="#">Section 3.3: SMPS</a> .
25-Oct-2019	5	<p>Introduced WLCSP100 package, hence updated <a href="#">Introduction</a>, <a href="#">Section 2: Reference board schematics</a> and <a href="#">Section 3.3: SMPS</a>. Updated <a href="#">Table 1: External components</a>.</p> <p>Updated <a href="#">Figure 8: UFQFPN48 reference board</a>, <a href="#">Figure 9: VFQFPN68 reference board</a>, <a href="#">Figure 19: 2-layer PCB - Reference boards for UFQFPN48, VFQFPN68 and UFBGA129</a>, <a href="#">Figure 21: 4-layer PCB - Reference board for WLCSP100</a>, <a href="#">Figure 22: PCB layout for UFQFPN48 (left to right: all, top and bottom layers)</a>, <a href="#">Figure 23: PCB layout for VFQFPN68 (left to right: all, top and bottom layers)</a>, <a href="#">Figure 25: PCB layout for WLCSP100</a>, <a href="#">Figure 26: Detail of PCB layout for the RF</a>, <a href="#">Figure 27: Detail of PCB layout for the SMPS</a> and <a href="#">Figure 28: Detail of PCB layout for the LSE</a>.</p> <p>Added <a href="#">Section 5.1: 2-layer PCB</a> and <a href="#">Section 5.2: 4-layer PCB</a>.</p> <p>Removed MB1355C board and related former <a href="#">Section 3: Nucleo board (MB1355C) schematics</a> and <a href="#">Section 6: 4-layer PCB Nucleo board MB1355C</a>.</p>
25-Jan-2020	6	<p>Introduced UFBGA129 package, hence updated <a href="#">Introduction</a>, <a href="#">Section 4.3: 2-layer PCB</a> and <a href="#">Section 6: Reference boards with IPD</a>.</p> <p>Updated <a href="#">Figure 8: UFQFPN48 reference board</a>, <a href="#">Figure 9: VFQFPN68 reference board</a>, <a href="#">Figure 11: WLCSP100 reference board</a>, <a href="#">Figure 26: Detail of PCB layout for the RF</a>, <a href="#">Figure 27: Detail of PCB layout for the SMPS</a> and <a href="#">Figure 28: Detail of PCB layout for the LSE</a>.</p> <p>Updated caption of <a href="#">Figure 19</a> and of <a href="#">Figure 21</a>.</p> <p>Added <a href="#">Figure 10: UFBGA129 reference board</a>, <a href="#">Figure 24: PCB layout for UFBGA129</a> and <a href="#">Figure 31: RF performance of the MLPF-WB55-02E3</a>.</p> <p>Added <a href="#">Table 5: References</a>.</p>

**IMPORTANT NOTICE – PLEASE READ CAREFULLY**

STMicroelectronics NV and its subsidiaries (“ST”) reserve the right to make changes, corrections, enhancements, modifications, and improvements to ST products and/or to this document at any time without notice. Purchasers should obtain the latest relevant information on ST products before placing orders. ST products are sold pursuant to ST’s terms and conditions of sale in place at the time of order acknowledgement.

Purchasers are solely responsible for the choice, selection, and use of ST products and ST assumes no liability for application assistance or the design of Purchasers’ products.

No license, express or implied, to any intellectual property right is granted by ST herein.

Resale of ST products with provisions different from the information set forth herein shall void any warranty granted by ST for such product.

ST and the ST logo are trademarks of ST. For additional information about ST trademarks, please refer to [www.st.com/trademarks](http://www.st.com/trademarks). All other product or service names are the property of their respective owners.

Information in this document supersedes and replaces information previously supplied in any prior versions of this document.

© 2020 STMicroelectronics – All rights reserved